

Primary School Motor Drivers 1

Geraldine Lee


geraldine343@gmail.com

Dr Mark Glickman

drmarkglickman@yahoo.com

Resistor Speed Controlled Motor

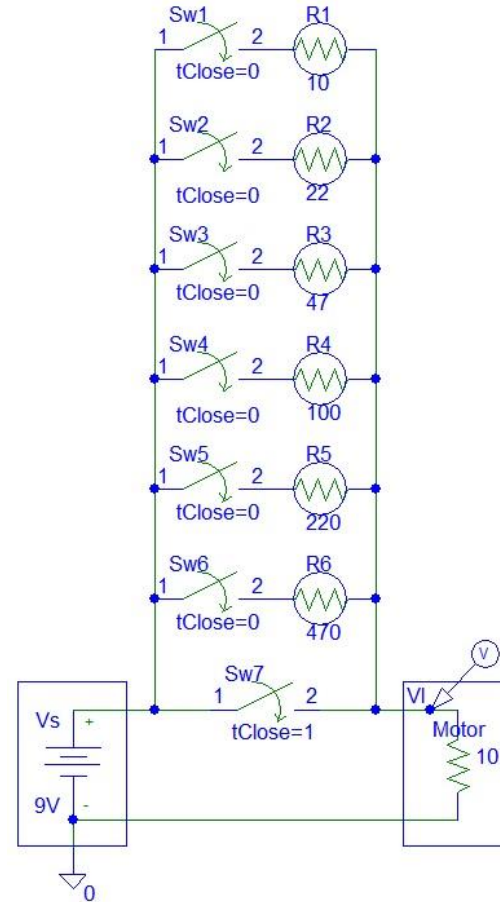- Higher resistor values cause the motor to rotate slowly.




Resistor Speed Controlled Motor


- Those high power resistors should be used for high power motors:




Variable Resistor Motor Driver Circuit

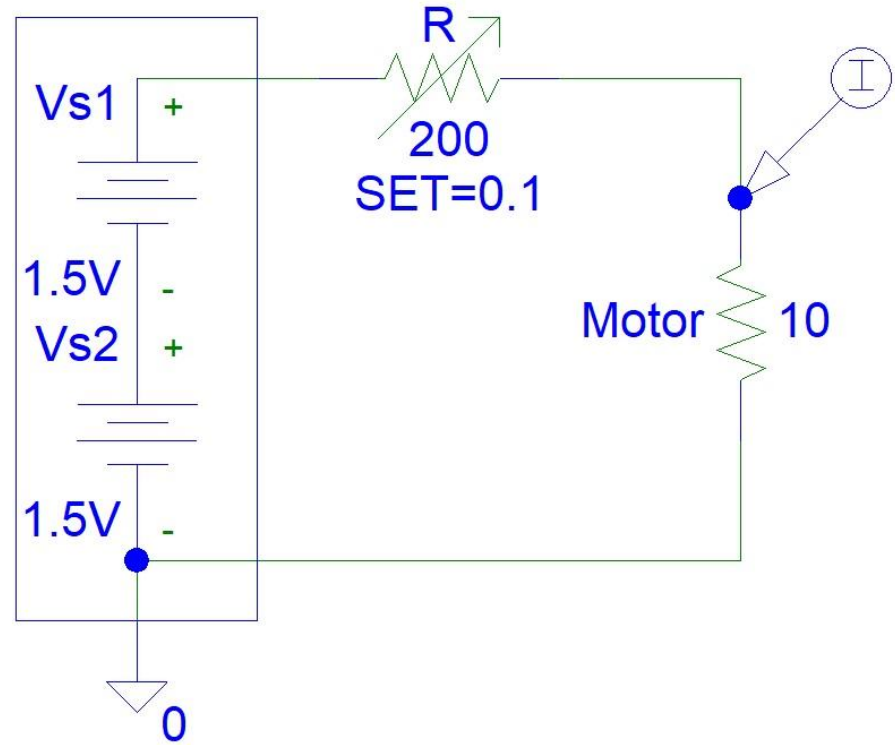

Variable Resistor Motor Driver Photos

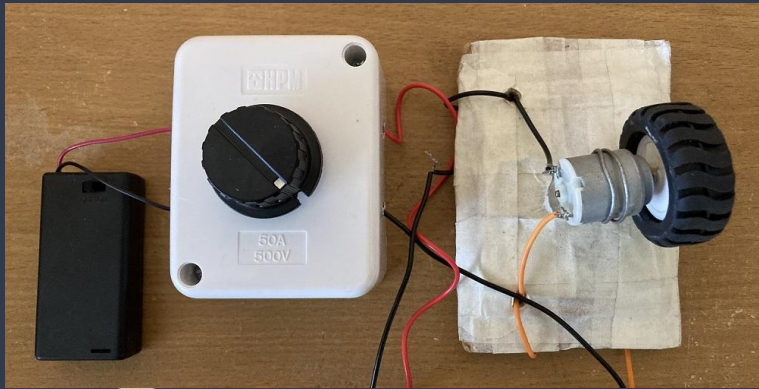

Variable Resistor Motor Driver Video

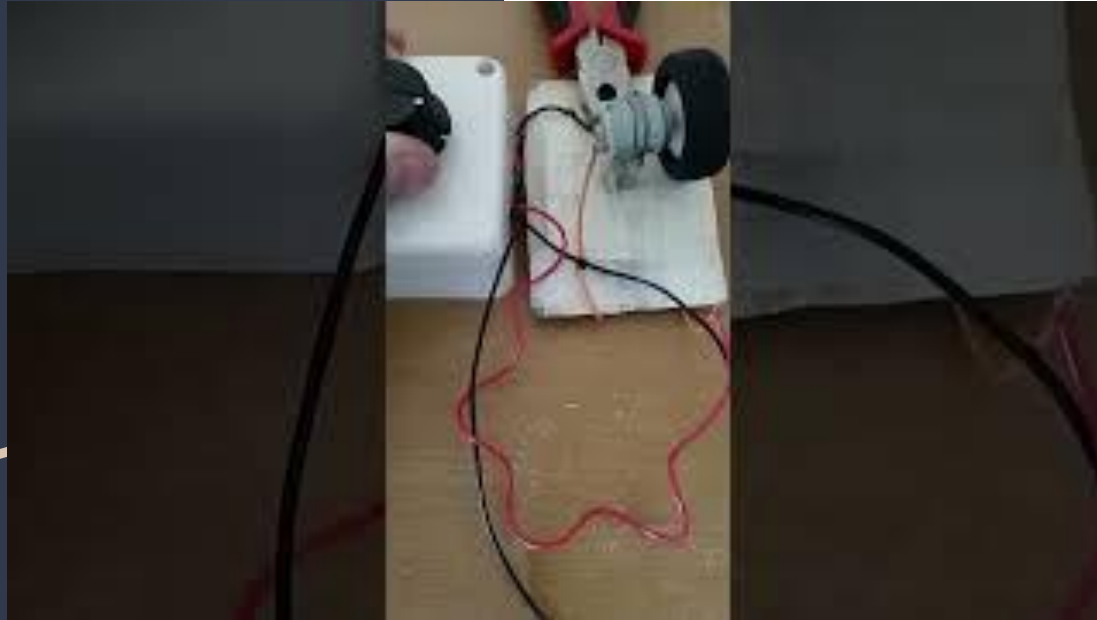

References

1. <https://instructables.com/member/diyelectronics>
2. <https://hackaday.io/diyelectronics>
3. <https://instructables.com/member/simplecircuits>
4. <https://hackaday.io/simplecircuits>
5. <https://instructables.com/member/simplecomponents>
6. <https://hackaday.io/simplecomponents>
7. <https://instructables.com/member/cheapcircuits>
8. <https://hackaday.io/cheapcircuits>
9. <https://instructables.com/member/supercircuits>
10. <https://hackaday.io/supercircuits>

References

1. <https://instructables.com/member/diycircuits>
2. <https://hackaday.io/diycircuits>
3. <https://instructables.com/member/usedcomponents>
4. <https://hackaday.io/usedcomponents>
5. <https://instructables.com/member/recycledcircuits>
6. <https://hackaday.io/recycledcircuits>
7. <https://instructables.com/member/recycledcomponents>
8. <https://hackaday.io/recycledcomponents>
9. <https://instructables.com/member/lowcostcircuits>
10. <https://hackaday.io/lowcostcircuits>